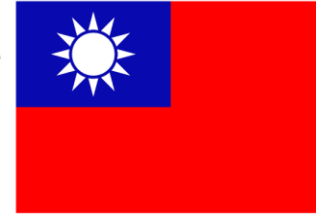




UNIVERSIDAD POLITÉCNICA  
TAIWAN – PARAGUAY  
臺灣-巴拉圭科技大學



# Boolean algebra fundamentals

# Fundamentals of Boolean Algebra

- Boolean algebra is defined with a set of *elements*, a set of *operators*, and a number of *axioms* and *postulates*.
- *A set of elements* is any collection of objects. If  $S$  is a set, and  $x$  and  $y$  are certain objects, then  $x \in S$  means that  $x$  is a member of the set  $S$  and  $y \notin S$  means that  $y$  is not an element of  $S$ .

# Fundamentals of Boolean Algebra

- **Basic Postulates**
- **Postulate 1 (Definition):** A Boolean algebra is a closed algebraic system containing a set  $K$  of two or more elements and the two operators  $\cdot$  and  $+$ . For every pair of elements of  $K$ , the binary operator specifies a rule for obtaining a unique element of  $K$ .
- **Postulate 2 (Existence of 1 and 0 element):**
  - (a)  $a + 0 = a$  (identity for  $+$ ),      (b)  $a \cdot 1 = a$  (identity for  $\cdot$ )
- **Postulate 3 (Commutativity):**
  - (a)  $a + b = b + a$ ,      (b)  $a \cdot b = b \cdot a$
- **Postulate 4 (Associativity):**
  - (a)  $a + (b + c) = (a + b) + c$       (b)  $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
- **Postulate 5 (Distributivity):**
  - (a)  $a + (b \cdot c) = (a + b) \cdot (a + c)$       (b)  $a \cdot (b + c) = a \cdot b + a \cdot c$
- **Postulate 6 (Existence of complement):**
  - (a)  $a + \bar{a} = 1$       (b)  $a \cdot \bar{a} = 0$

Precedence

()

'

$\cdot$

$+$

Note: Normally  $\cdot$  is omitted.

# Fundamentals of Boolean Algebra

- **Fundamental Theorems of Boolean Algebra**

- **Theorem 1 (Idempotency):**

(a)  $a + a = a$

(b)  $aa = a$

- **Theorem 2 (Null element):**

(a)  $a + 1 = 1$

(b)  $a0 = 0$

- **Theorem 3 (Involution)**

$$\overline{\overline{a}} = a$$

- **Properties of 0 and 1 elements:**

OR

AND

Complement

$$a + 0 = a$$

$$a0 = 0$$

$$0' = 1$$

$$a + 1 = 1$$

$$a1 = a$$

$$1' = 0$$

# Fundamentals of Boolean Algebra

- **Theorem 4 (Absorption)**

(a)  $a + ab = a$

(b)  $a(a + b) = a$

- **Examples:**

- $(X + Y) + (X + Y)Z = X + Y$  [T4(a)]

- $AB'(AB' + B'C) = AB'$  [T4(b)]

- **Theorem 5**

(a)  $a + a'b = a + b$

(b)  $a(a' + b) = ab$

- **Examples:**

- $B + AB'C'D = B + AC'D$  [T5(a)]

- $(X + Y)((X + Y)' + Z) = (X + Y)Z$  [T5(b)]

# Fundamentals of Boolean Algebra

- **Theorem 6**

(a)  $ab + ab' = a$

(b)  $(a + b)(a + b') = a$

- **Examples:**

- $ABC + AB'C = AC$  [T6(a)]

- $(W' + X' + Y' + Z')(W' + X' + Y' + Z)(W' + X' + Y + Z')(W' + X' + Y + Z)$

$= (W' + X' + Y')(W' + X' + Y + Z')(W' + X' + Y + Z)$  [T6(b)]

$= (W' + X' + Y')(W' + X' + Y)$  [T6(b)]

$= (W' + X')$  [T6(b)]

# Fundamentals of Boolean Algebra

- **Theorem 7**

$$(a) \quad ab + ab'c = ab + ac$$

$$(b) \quad (a + b)(a + b' + c) = (a + b)(a + c)$$

- **Examples:**

- $wy' + wx'y + wxyz + wxz' = wy' + wx'y + wxy + wxz'$  [T7(a)]

$$= wy' + wy + wxz'$$
 [T7(a)]

$$= w + wxz'$$
 [T7(a)]

$$= w$$
 [T7(a)]

- $(x'y' + z)(w + x'y' + z') = (x'y' + z)(w + x'y')$  [T7(b)]

# Fundamentals of Boolean Algebra

- **Theorem 8 (DeMorgan's Theorem)**

$$(a) (a + b)' = a'b' \qquad (b) (ab)' = a' + b'$$

- Generalized DeMorgan's Theorem

$$(a) (a + b + \dots z)' = a'b' \dots z' \qquad (b) (ab \dots z)' = a' + b' + \dots z'$$

- **Examples:**

$$\begin{aligned} \bullet (a + bc)' &= (a + (bc))' && [T8(a)] \\ &= a'(bc)' && [T8(b)] \\ &= a'(b' + c') && [P5(b)] \\ &= a'b' + a'c' \end{aligned}$$

- Note:  $(a + bc)' \neq a'b' + c'$



# Fundamentals of Boolean Algebra

- **More Examples for DeMorgan's Theorem**

- $(a(b + z(x + a'))))' = a' + (b + z(x + a'))'$  [T8(b)]  
 $= a' + b' (z(x + a'))'$  [T8(a)]  
 $= a' + b' (z' + (x + a'))'$  [T8(b)]  
 $= a' + b' (z' + x'(a'))'$  [T8(a)]  
 $= a' + b' (z' + x'a)$  [T3]  
 $= a' + b' (z' + x')$  [T5(a)]

- $(a(b + c) + a'b)' = (ab + ac + a'b)'$  [P5(b)]  
 $= (b + ac)'$  [T6(a)]  
 $= b'(ac)'$  [T8(a)]  
 $= b'(a' + c')$  [T8(b)]

# Fundamentals of Boolean Algebra

***Apply DeMorgan's Theorem to these expressions***

- $(X+Y+Z)'$
- $(PQ+R)'$
- $(M+N)'Q'$

# Fundamentals of Boolean Algebra

- **Theorem 9 (Consensus)**

$$(a) \quad ab + a'c + bc = ab + a'c \qquad (b) \quad (a + b)(a' + c)(b + c) = (a + b)(a' + c)$$

- **Examples:**

$$\bullet \quad AB + A'CD + BCD = AB + A'CD \qquad [T9(a)]$$

$$\bullet \quad (a + b')(a' + c)(b' + c) = (a + b')(a' + c) \qquad [T9(b)]$$

$$\bullet \quad ABC + A'D + B'D + CD = ABC + (A' + B')D + CD \qquad [P5(b)]$$

$$= ABC + (AB)'D + CD \qquad [T8(b)]$$

$$= ABC + (AB)'D \qquad [T9(a)]$$

$$= ABC + (A' + B')D \qquad [T8(b)]$$

$$= ABC + A'D + B'D \qquad [P5(b)]$$

# Switching Functions

- **Switching algebra:** Boolean algebra with the set of elements  $K = \{0, 1\}$   
If there are  $n$  variables, we can define  $2^{2^n}$  switching functions.
- Sixteen functions of two variables:

| AB | $f_0$ | $f_1$ | $f_2$ | $f_3$ | $f_4$ | $f_5$ | $f_6$ | $f_7$ | $f_8$ | $f_9$ | $f_{10}$ | $f_{11}$ | $f_{12}$ | $f_{13}$ | $f_{14}$ | $f_{15}$ |
|----|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|----------|----------|----------|----------|----------|----------|
| 00 | 0     | 1     | 0     | 1     | 0     | 1     | 0     | 1     | 0     | 1     | 0        | 1        | 0        | 1        | 0        | 1        |
| 01 | 0     | 0     | 1     | 1     | 0     | 0     | 1     | 1     | 0     | 0     | 1        | 1        | 0        | 0        | 1        | 1        |
| 10 | 0     | 0     | 0     | 0     | 1     | 1     | 1     | 1     | 0     | 0     | 0        | 0        | 1        | 1        | 1        | 1        |
| 11 | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 0     | 1     | 1     | 1        | 1        | 1        | 1        | 1        | 1        |

- A switching function can be represented by a table as above, or by a switching expression as follows:

$$f_0(A,B)=0, f_6(A,B) = AB' + A'B, f_{11}(A,B) = AB + A'B + A'B' = A' + B, \dots$$

- Value of a function can be obtained by plugging in the values of all variables:  
The value of  $f_6$  when  $A = 1$  and  $B = 0$  is:  $1 \cdot 0' + 1' \cdot 0 = 0 + 1 = 1$ .

# Truth Tables

- Shows the value of a function for all possible input combinations.
- Truth tables for OR, AND, and NOT:

| $ab$ | $f(a,b)=a+b$ | $ab$ | $f(a,b)=ab$ | $a$ | $f(a)=a'$ |
|------|--------------|------|-------------|-----|-----------|
| 00   | 0            | 00   | 0           | 0   | 1         |
| 01   | 1            | 01   | 0           | 1   | 0         |
| 10   | 1            | 10   | 0           |     |           |
| 11   | 1            | 11   | 1           |     |           |

# Truth Tables

- Truth tables for  $f(A,B,C) = AB + A'C + AC'$

| $ABC$ | $f(A,B,C)$ | $ABC$      | $f(A,B,C)$ |
|-------|------------|------------|------------|
| 000   | 0          | <i>FFF</i> | <i>F</i>   |
| 001   | 1          | <i>FFT</i> | <i>T</i>   |
| 010   | 0          | <i>FTF</i> | <i>F</i>   |
| 011   | 1          | <i>FTT</i> | <i>T</i>   |
| 100   | 1          | <i>TFF</i> | <i>T</i>   |
| 101   | 0          | <i>TFT</i> | <i>F</i>   |
| 110   | 1          | <i>TTF</i> | <i>T</i>   |
| 111   | 1          | <i>TTT</i> | <i>T</i>   |

# Algebraic Forms of Switching Functions

- ***Literal***: A variable, complemented or uncomplemented.
- ***Product term***: A literal or literals ANDed together.
- ***Sum term***: A literal or literals ORed together.
  
- ***SOP (Sum of Products)***:
  - ORing product terms
  - $f(A, B, C) = ABC + A'C + B'C$
  
- ***POS (Product of Sums)***:
  - ANDing sum terms
  - $f(A, B, C) = (A' + B' + C')(A + C')(B + C')$

# Algebraic Forms of Switching Functions

- A *minterm* is a **product** term in which all the variables appear exactly once either complemented or uncomplemented.
- **Canonical Sum of Products (canonical SOP):**
  - Represented as a sum of minterms only.
  - **Example:**  $f_1(A,B,C) = A'BC' + ABC' + A'BC + ABC$
- Minterms of three variables:

| Minterm  | Minterm Code | Minterm Number |
|----------|--------------|----------------|
| $A'B'C'$ | 000          | $m_0$          |
| $A'B'C$  | 001          | $m_1$          |
| $A'BC'$  | 010          | $m_2$          |
| $A'BC$   | 011          | $m_3$          |
| $AB'C'$  | 100          | $m_4$          |
| $AB'C$   | 101          | $m_5$          |
| $ABC'$   | 110          | $m_6$          |
| $ABC$    | 111          | $m_7$          |



# Algebraic Forms of Switching Functions

- Compact form of canonical SOP form:

$$f_1(A,B,C) = m_2 + m_3 + m_6 + m_7$$

- A further simplified form:

$$f_1(A,B,C) = \Sigma m (2,3,6,7) \text{ (minterm list form)}$$

- The ***order of variables*** in the functional notation is important.
- Deriving truth table of  $f_1(A,B,C)$  from minterm list:

| Row No.<br>(i) | Inputs<br>$ABC$ | Outputs<br>$f_1(A,B,C) = \Sigma m(2,3,6,7)$ | Complement<br>$f_1'(A,B,C) = \Sigma m(0,1,4,5)$ |
|----------------|-----------------|---|---|
| 0              | 000             | 0   | 1 $\leftarrow m_0$                              |
| 1              | 001             | 0   | 1 $\leftarrow m_1$                              |
| 2              | 010             | 1 $\leftarrow m_2$                          | 0   |
| 3              | 011             | 1 $\leftarrow m_3$                          | 0   |
| 4              | 100             | 0   | 1 $\leftarrow m_4$                              |
| 5              | 101             | 0   | 1 $\leftarrow m_5$                              |
| 6              | 110             | 1 $\leftarrow m_6$                          | 0   |
| 7              | 111             | 1 $\leftarrow m_7$                          | 0   |

# Algebraic Forms of Switching Functions

- **Example:** Given  $f(A,B,Q,Z) = A'B'Q'Z' + A'B'Q'Z + A'BQZ' + A'BQZ$ , express  $f(A,B,Q,Z)$  and  $f'(A,B,Q,Z)$  in minterm list form.

$$\begin{aligned}f(A,B,Q,Z) &= A'B'Q'Z' + A'B'Q'Z + A'BQZ' + A'BQZ \\&= m_0 + m_1 + m_6 + m_7 \\&= \Sigma m(0, 1, 6, 7)\end{aligned}$$

$$\begin{aligned}f'(A,B,Q,Z) &= m_2 + m_3 + m_4 + m_5 + m_8 + m_9 + m_{10} + m_{11} + m_{12} \\&\quad + m_{13} + m_{14} + m_{15} \\&= \Sigma m(2, 3, 4, 5, 8, 9, 10, 11, 12, 13, 14, 15)\end{aligned}$$

- $\sum_{i=0}^{2^n-1} m_i = 1$  (2.6)
- $AB + (AB)' = 1$  and  $AB + A' + B' = 1$ , but  $AB + A'B' \neq 1$ .

# Algebraic Forms of Switching Functions

- A *maxterm* is a **sum** term in which all the variables appear exactly once either complemented or uncomplemented.
- **Canonical Product of Sums (canonical POS):**
  - Represented as a product of maxterms only.
  - **Example:**  $f_2(A,B,C) = (A+B+C)(A+B+C')(A'+B+C)(A'+B+C')$
- Maxterms of three variables:

| Maxterm    | Maxterm Code | Maxterm Number |
|------------|--------------|----------------|
| $A+B+C$    | 000          | $M_0$          |
| $A+B+C'$   | 001          | $M_1$          |
| $A+B'+C$   | 010          | $M_2$          |
| $A+B'+C'$  | 011          | $M_3$          |
| $A'+B+C$   | 100          | $M_4$          |
| $A'+B+C'$  | 101          | $M_5$          |
| $A'+B'+C$  | 110          | $M_6$          |
| $A'+B'+C'$ | 111          | $M_7$          |

# Algebraic Forms of Switching Functions

- $f_2(A,B,C) = M_0M_1M_4M_5$   
 $= \Pi M(0,1,4,5)$  (maxterm list form)

- The truth table for  $f_2(A,B,C)$ :

| Rwo No.<br>(i) | Inputs<br>$ABC$ | $M_0$<br>$A+B+C$ | $M_1$<br>$A+B+C'$ | $M_4$<br>$A'+B+C$ | $M_5$<br>$A'+B+C'$ | Outputs<br>$f_2(A,B,C)$ |
|----------------|-----------------|------------------|-------------------|-------------------|--------------------|-------------------------|
| 0              | 000             | 0                | 1                 | 1                 | 1                  | 0                       |
| 1              | 001             | 1                | 0                 | 1                 | 1                  | 0                       |
| 2              | 010             | 1                | 1                 | 1                 | 1                  | 1                       |
| 3              | 011             | 1                | 1                 | 1                 | 1                  | 1                       |
| 4              | 100             | 1                | 1                 | 0                 | 1                  | 0                       |
| 5              | 101             | 1                | 1                 | 1                 | 0                  | 0                       |
| 6              | 110             | 1                | 1                 | 1                 | 1                  | 1                       |
| 7              | 111             | 1                | 1                 | 1                 | 1                  | 1                       |

# Algebraic Forms of Switching Functions

- Truth tables of  $f_1(A,B,C)$  and  $f_2(A,B,C)$  are identical.

- Hence,  $f_1(A,B,C) = \sum m(2,3,6,7)$   

$$= f_2(A,B,C)$$
  

$$= \prod M(0,1,4,5)$$

- **Example:** Given  $f(A,B,C) = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C')$ , construct the truth table and express in both maxterm and minterm form.

- $f(A,B,C) = M_1M_3M_5M_7 = \prod M(1,3,5,7) = \sum m(0,2,4,6)$

| Row No.<br>(i) | Inputs<br>ABC | Outputs<br>$f(A,B,C) = \prod M(1,3,5,7) = \sum m(0,2,4,6)$ |
|----------------|---------------|--|
| 0              | 000           | 1 <span style="float:right"><math>m_0</math></span>        |
| 1              | 001           | 0 $\leftarrow M_1$   |
| 2              | 010           | 1 <span style="float:right"><math>m_2</math></span>        |
| 3              | 011           | 0 $\leftarrow M_3$   |
| 4              | 100           | 1 <span style="float:right"><math>m_4</math></span>        |
| 5              | 101           | 0 $\leftarrow M_5$   |
| 6              | 110           | 1 <span style="float:right"><math>m_6</math> 21</span>     |
| 7              | 111           | 0 $\leftarrow M_7$   |

# Algebraic Forms of Switching Functions

- Relationship between minterm  $m_i$  and maxterm  $M_i$ :
  - For  $f(A,B,C)$ ,  $(m_1)' = (A'B'C)' = A + B + C' = M_1$
  - In general,  $(m_i)' = M_i$   
 $(M_i)' = ((m_i)')' = m_i$

# Algebraic Forms of Switching Functions

- **Example:** Relationship between the maxterms for a function and its complement.
  - For  $f(A,B,C) = (A+B+C')(A+B'+C')(A'+B+C')(A'+B'+C')$
  - The truth table is:

| Row No.<br>(i) | Inputs<br>$ABC$ | Outputs<br>$f(A,B,C)$ | Outputs<br>$f'(A,B,C) = \prod M(0,2,4,6)$ |
|----------------|-----------------|-----------------------|---|
| 0              | 000             | 1                     | 0 $\leftarrow M_0$                        |
| 1              | 001             | 0                     | 1   |
| 2              | 010             | 1                     | 0 $\leftarrow M_2$                        |
| 3              | 011             | 0                     | 1   |
| 4              | 100             | 1                     | 0 $\leftarrow M_4$                        |
| 5              | 101             | 0                     | 1   |
| 6              | 110             | 1                     | 0 $\leftarrow M_6$                        |
| 7              | 111             | 0                     | 1   |

# Algebraic Forms of Switching Functions

- From the truth table

$$f'(A,B,C) = \prod M(0,2,4,6) \text{ and } f(A,B,C) = \prod M(1,3,5,7)$$

- Since  $f(A,B,C) \cdot f'(A,B,C) = 0$ ,  
 $(M_0 M_2 M_4 M_6)(M_1 M_3 M_5 M_7) = 0$  or  $\prod_{i=0}^{2^3-1} M_i = 0$
- In general,  $\prod_{i=0}^{2^n-1} M_i = 0$

- Another observation from the truth table:

$$f(A,B,C) = \sum m(0,2,4,6) = \prod M(1,3,5,7)$$

$$f'(A,B,C) = \sum m(1,3,5,7) = \prod M(0,2,4,6)$$



# Derivation of Canonical Forms

- Derive canonical POS or SOP using switching algebra.

- **Theorem 10. Shannon's expansion theorem**

- (a).  $f(x_1, x_2, \dots, x_n) = x_1 f(1, x_2, \dots, x_n) + (x_1)' f(0, x_2, \dots, x_n)$

- (b).  $f(x_1, x_2, \dots, x_n) = [x_1 + f(0, x_2, \dots, x_n)] [(x_1)' + f(1, x_2, \dots, x_n)]$

- **Example:**  $f(A,B,C) = AB + AC' + A'C$

- $f(A,B,C) = AB + AC' + A'C = A f(1,B,C) + A' f(0,B,C)$

- $= A(1 \cdot B + 1 \cdot C' + 1' \cdot C) + A'(0 \cdot B + 0 \cdot C' + 0' \cdot C) = A(B + C') + A'C$

- $f(A,B,C) = A(B + C') + A'C = B[A(1+C') + A'C] + B'[A(0 + C') + A'C]$

- $= B[A + A'C] + B'[AC' + A'C] = AB + A'BC + AB'C' + A'B'C$

- $f(A,B,C) = AB + A'BC + AB'C' + A'B'C$

- $= C[AB + A'B \cdot 1 + AB' \cdot 1' + A'B' \cdot 1] + C'[AB + A'B \cdot 0 + AB' \cdot 0' + A'B' \cdot 0]$

- $= ABC + A'BC + A'B'C + ABC' + AB'C'$

# Derivation of Canonical Forms

- **Alternative:** Use Theorem 6 to add missing literals.
- **Example:**  $f(A,B,C) = AB + AC' + A'C$  to canonical SOP form.
  - $AB = ABC' + ABC = m_6 + m_7$
  - $AC' = AB'C' + ABC' = m_4 + m_6$
  - $A'C = A'B'C + A'BC = m_1 + m_3$
  - Therefore,
$$f(A,B,C) = (m_6 + m_7) + (m_4 + m_6) + (m_1 + m_3) = \Sigma m(1, 3, 4, 6, 7)$$
- **Example:**  $f(A,B,C) = A(A + C')$  to canonical POS form.
  - $A = (A+B')(A+B) = (A+B'+C')(A+B'+C)(A+B+C')(A+B+C)$ 
$$= M_3 M_2 M_1 M_0$$
  - $(A+C') = (A+B'+C')(A+B+C') = M_3 M_1$
  - Therefore,
$$f(A,B,C) = (M_3 M_2 M_1 M_0)(M_3 M_1) = \Pi M(0, 1, 2, 3)$$

# Incompletely Specified Functions

- A switching function may be incompletely specified.
- Some minterms are omitted, which are called *don't-care minterms*.
- Don't cares arise in two ways:
  - Certain input combinations never occur.
  - Output is required to be 1 or 0 only for certain combinations.
- Don't care minterms:  $d_i$                       Don't care maxterms:  $D_i$
- **Example:**  $f(A,B,C)$  has minterms  $m_0, m_3$ , and  $m_7$  and don't-cares  $d_4$  and  $d_5$ .
  - Minterm list is:  $f(A,B,C) = \sum m(0,3,7) + d(4,5)$
  - Maxterm list is:  $f(A,B,C) = \prod M(1,2,6) \cdot D(4,5)$
  - $f'(A,B,C) = \sum m(1,2,6) + d(4,5) = \prod M(0,3,7) \cdot D(4,5)$
  - $f(A,B,C) = A'B'C' + A'BC + ABC + d(AB'C' + AB'C)$   
 $= B'C' + BC$  (use  $d_4$  and omit  $d_5$ )


# Electronic Logic Gates

- ***Electrical Signals and Logic Values***


| Electric Signal  | Logic Value    |                |
|------------------|----------------|----------------|
|                  | Positive Logic | Negative Logic |
| High Voltage (H) | 1              | 0              |
| Low Voltage (L)  | 0              | 1              |

- A signal that is set to logic 1 is said to be *asserted*, *active*, or *true*.
- An *active-high* signal is asserted when it is high (positive logic).
- An *active-low* signal is asserted when it is low (negative logic).

# Electronic Logic Gates

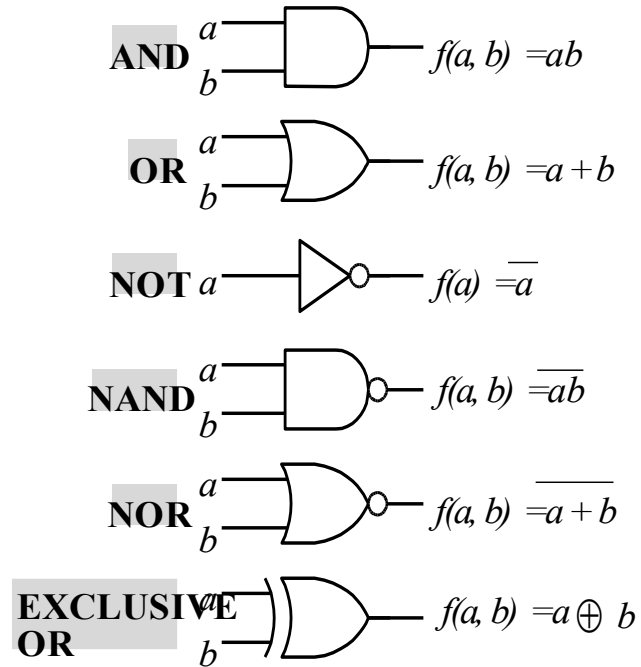


Symbol set 1

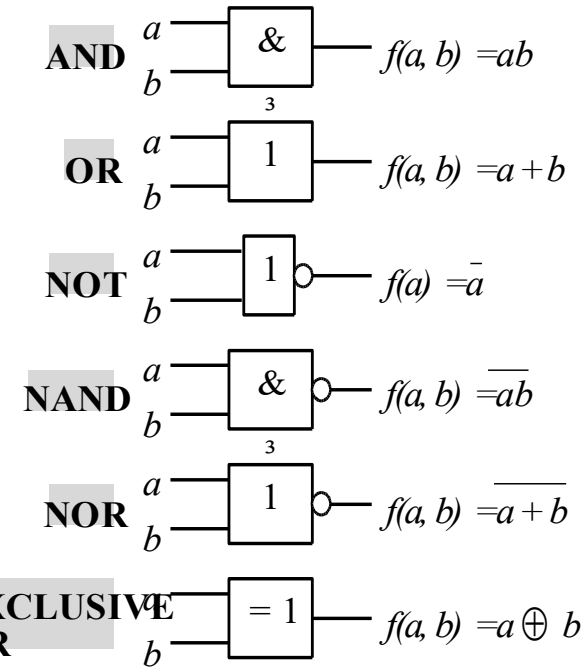


Symbol set 2

(ANSI/IEEE Standard 91-1984)


# Electronic Logic Gates

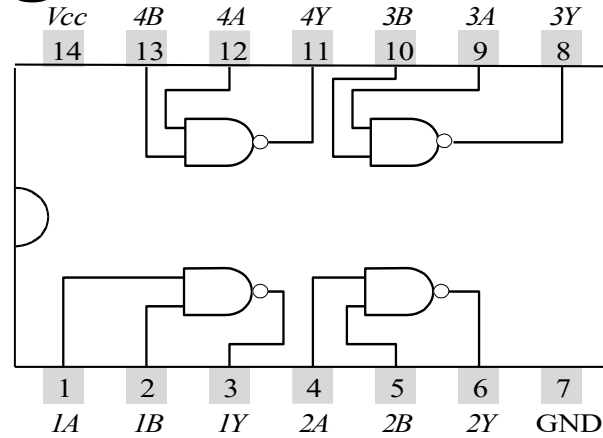

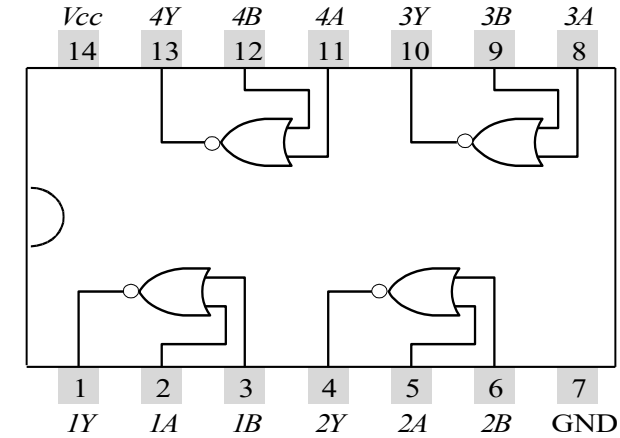
$7400Y = \overline{AB}$   
Quadruple two-input NAND gates



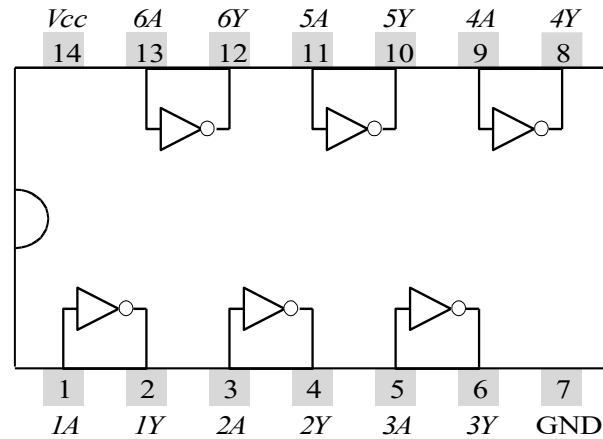$7402Y = \overline{A+B}$   
Quadruple two-input NOR gates




$7404Y = \overline{A}$   
Hex inverters

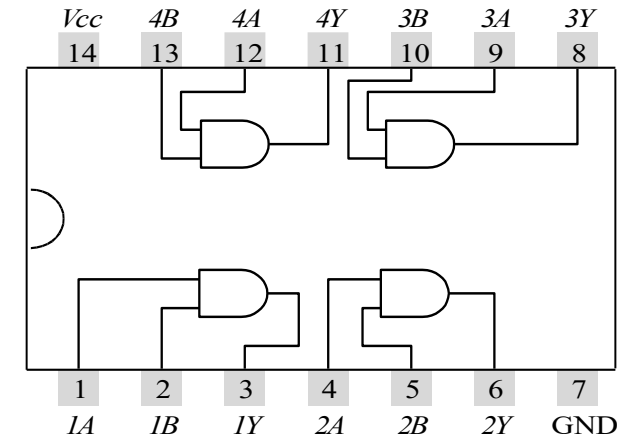


$7408Y = AB$   
Quadruple two-input AND gates

# Electronic Logic Gates

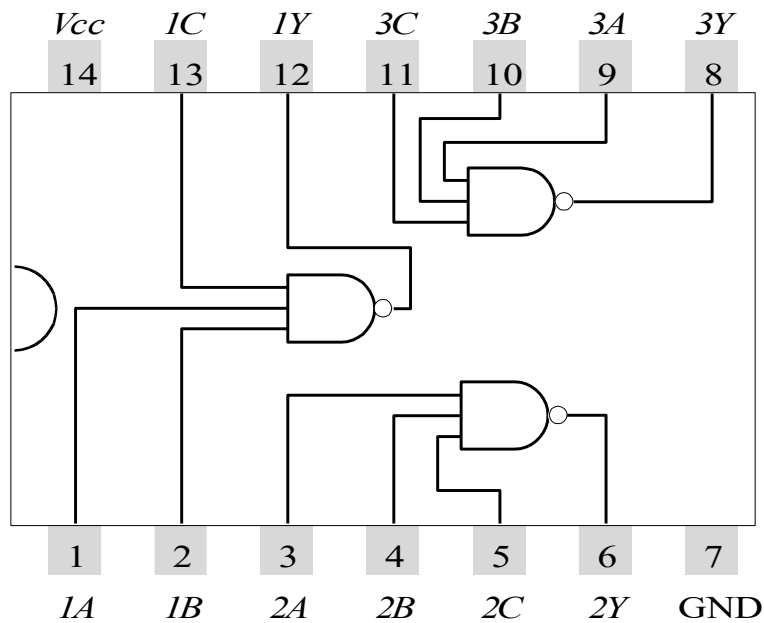


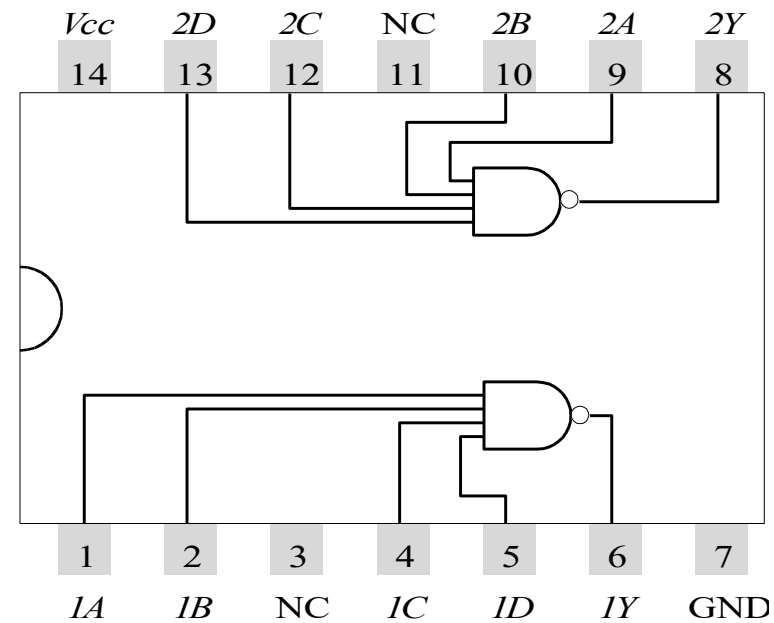7410  $Y = \overline{ABC}$   
Triple three-input NAND gates




7420  $Y = \overline{ABCD}$   
Dual four-input NAND gates


# Electronic Logic Gates

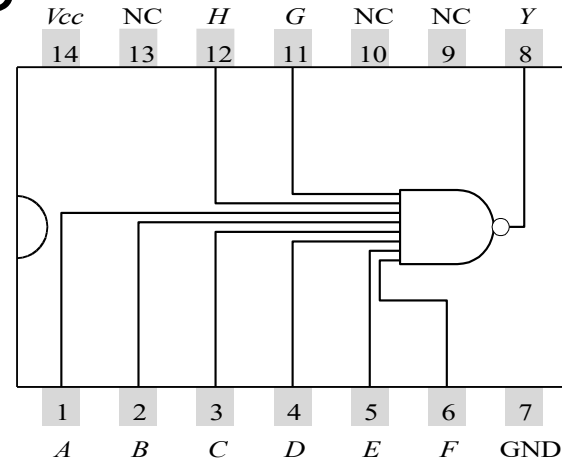

$7430Y = ABCDEFGH$   
8-input NAND gate

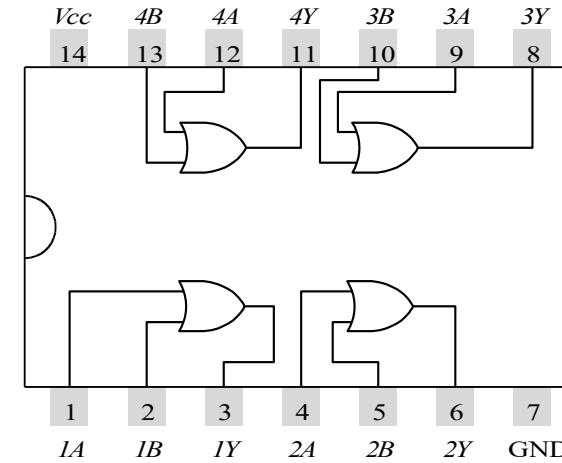

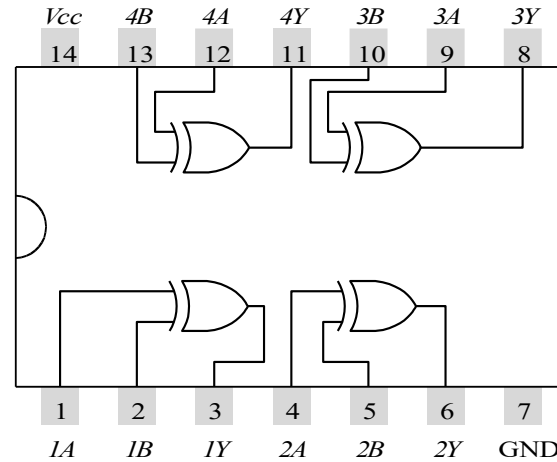$7432Y = A + B$   
Quadrate two-input OR gates



$7486Y = A \oplus B$   
Quadrate two-input exclusive-OR gates



# Basic Functional Components


- **AND**

| $a$ | $b$ | $f_{AND}(a, b) = ab$ |
|-----|-----|----------------------|
| 0   | 0   | 0                    |
| 0   | 1   | 0                    |
| 1   | 0   | 0                    |
| 1   | 1   | 1                    |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | L   |
| L   | H   | L   |
| H   | L   | L   |
| H   | H   | H   |

(b)

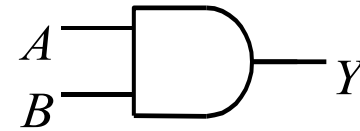

(c)

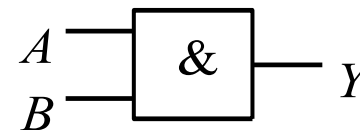

(d)

- (a) AND logic function.
- (b) Electronic AND gate.
- (c) Standard symbol.
- (d) IEEE block symbol.

# Basic Functional Components


- **OR**

| $a$ | $b$ | $f_{OR}(a, b) = a + b$ |
|-----|-----|------------------------|
| 0   | 0   | 0                      |
| 0   | 1   | 1                      |
| 1   | 0   | 1                      |
| 1   | 1   | 1                      |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | L   |
| L   | H   | H   |
| H   | L   | H   |
| H   | H   | H   |

(b)

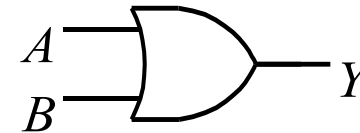

(c)

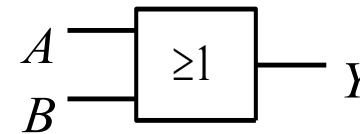

(d)

- (a) OR logic function.
- (b) Electronic OR gate.
- (c) Standard symbol.
- (d) IEEE block symbol.

# Basic Functional Components

- Meaning of the designation  $\geq 1$  in IEEE symbol:

| $ab$ | $\text{sum}(a, b)$ | $\text{sum}(a, b) \geq 1$ | $f_{OR}(a, b) = a + b$ |
|------|--------------------|---------------------------|------------------------|
| 00   | 0                  | False                     | 0                      |
| 01   | 1                  | True                      | 1                      |
| 10   | 1                  | True                      | 1                      |
| 11   | 2                  | True                      | 1                      |

# Basic Functional Components (4)


- **NOT**

| $a$ | $fNOT(a) = \bar{a}$ |
|-----|---------------------|
| 0   | 1                   |
| 1   | 0                   |


(a)

| $A$ | $Y$ |
|-----|-----|
| L   | H   |
| H   | L   |

(b)

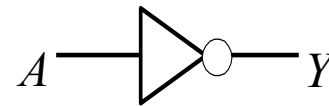

(c)

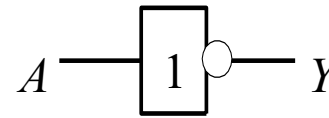

(d)

- (a) NOT logic function.
- (b) Electronic NOT gate.
- (c) Standard symbol.
- (d) IEEE block symbol.

# Basic Functional Components

- ***Positive Versus Negative Logic***



|                     | Positive Logic | Negative Logic |
|---------------------|----------------|----------------|
| 1 is represented by | High Voltage   | Low Voltage    |
| 0 is represented by | Low Voltage    | High Voltage   |

# Basic Functional Components

- **AND Gate Usage in Negative Logic**

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| 1   | 1   | 1   |
| 1   | 0   | 1   |
| 0   | 1   | 1   |
| 0   | 0   | 0   |

(a)

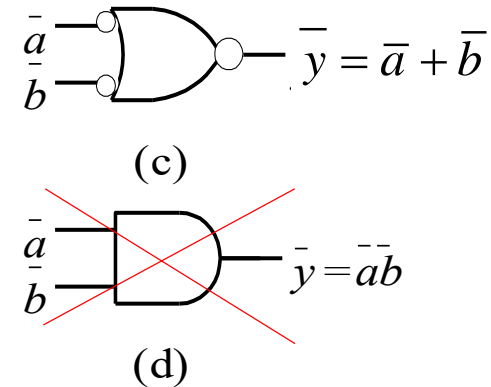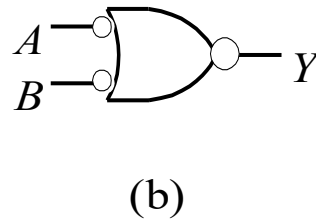




- (a) AND gate truth table ( $L = 1, H = 0$ )
- (b) Alternate AND gate symbol (in negative logic)
- (c) Preferred usage  $y = a \cdot b = \overline{\overline{a} + \overline{b}} = \overline{\overline{a} + \overline{b}} = \overline{f_{OR}(\overline{a}, \overline{b})}$
- (d) Improper usage  $\overline{y} = \overline{(\overline{a}) + (\overline{b})} = \overline{a + b} = \overline{f_{OR}(a, b)}$

# Basic Functional Components

- **OR Gate Usage in Negative Logic**

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| 1   | 1   | 1   |
| 1   | 0   | 0   |
| 0   | 1   | 0   |
| 0   | 0   | 0   |

(a)

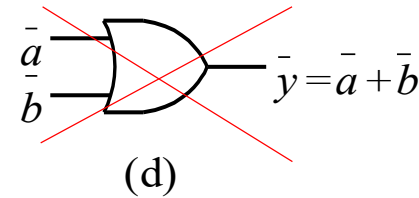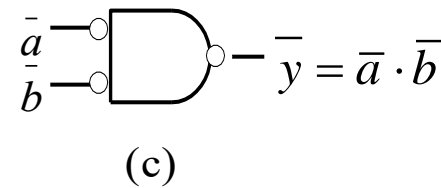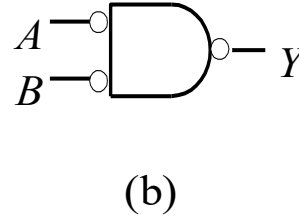

- (a) OR gate truth table ( $L = 1, H = 0$ )
- (b) Alternate OR gate symbol (in negative logic)
- (c) Preferred usage  $y = a + b = \overline{\overline{a + b}} = \overline{\overline{a} \cdot \overline{b}} = \bar{f}_{AND}(\bar{a}, \bar{b})$
- (d) Improper usage  $\bar{y} = \overline{(\overline{a}) \cdot (\overline{b})} = \overline{a \cdot b} = \bar{f}_{AND}(a, b)$

# Basic Functional Components


- **NAND**

| $a$ | $b$ | $f_{NAND}(a, b) = \overline{ab}$ |
|-----|-----|----------------------------------|
| 0   | 0   | 1                                |
| 0   | 1   | 1                                |
| 1   | 0   | 1                                |
| 1   | 1   | 0                                |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | H   |
| L   | H   | H   |
| H   | L   | H   |
| H   | H   | L   |


(b)

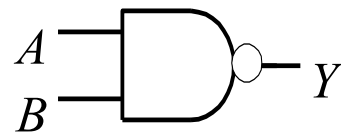

(c)

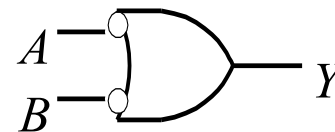

(d)

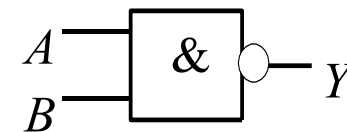

(e)



- (a) NAND logic function
- (b) Electronic NAND gate
- (c) Standard symbol
- (e) IEEE block symbol



# Basic Functional Components

- Matching signal polarity to NAND gate inputs/outputs

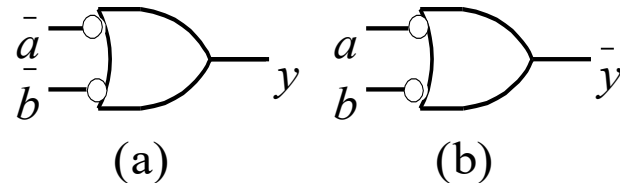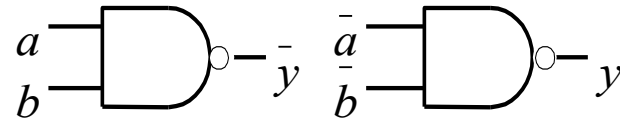- (a) Preferred usage
  - (b) Improper usage



- Additional properties of NAND gate:

$$f_{NAND}(a, a) = \overline{a \cdot a} = \bar{a} = f_{NOT}(a)$$


$$\bar{f}_{NAND}(a, b) = \overline{\overline{a \cdot b}} = a \cdot b = f_{AND}(a, b)$$

$$f_{NAND}(\bar{a}, \bar{b}) = \overline{\bar{a} \cdot \bar{b}} = a + b = f_{OR}(a, b)$$

- Hence, NAND gate may be used to implement all three elementary operators.

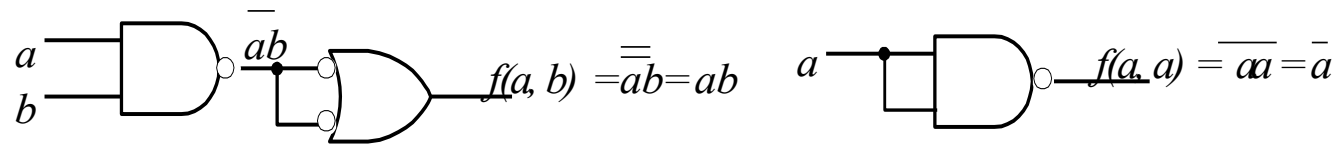
# Basic Functional Components

- AND, OR, and NOT gates constructed exclusively from NAND gates



**AND gate**

**NOT gate**

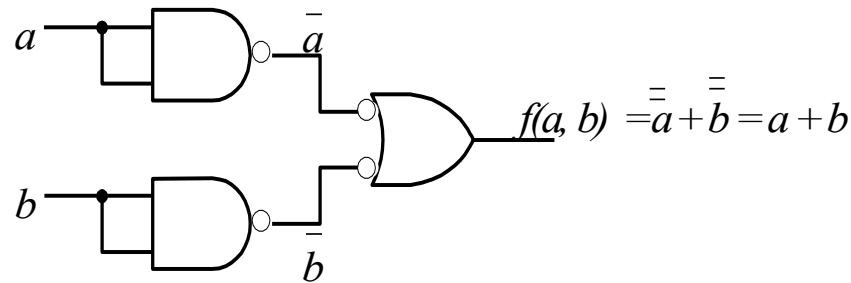

**OR gate**

# Basic Functional Components


- **NOR**

| $a$ | $b$ | $f_{NOR}(a, b) = \overline{a + b}$ |
|-----|-----|------------------------------------|
| 0   | 0   | 1                                  |
| 0   | 1   | 0                                  |
| 1   | 0   | 0                                  |
| 1   | 1   | 0                                  |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | H   |
| L   | H   | L   |
| H   | L   | L   |
| H   | H   | L   |


(b)

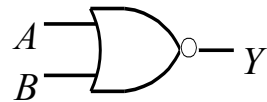

(c)

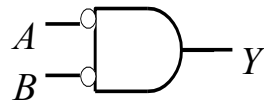

(d)

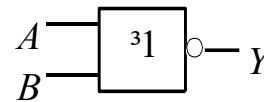


(e)

- (a) NAND logic function
- (b) Electronic NAND gate
- (c) Standard symbol
- (d) IEEE block symbol

# Basic Functional Components

- Matching signal polarity to NOR gate inputs/outputs

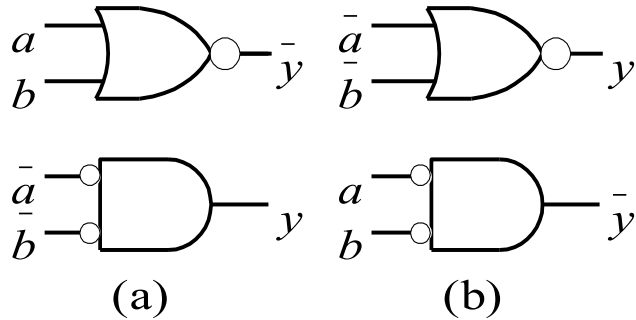- (a) Preferred usage
  - (b) Improper usage



- Additional properties of NOR gate:

$$f_{NOR}(a, a) = \overline{a + a} = \bar{a} = f_{NOT}(a)$$


$$\overline{f_{NOR}(a, b)} = \overline{\overline{a + b}} = a + b = f_{OR}(a, b)$$

$$f_{NOR}(\bar{a}, \bar{b}) = \overline{\bar{a} + \bar{b}} = a \cdot b = f_{AND}(a, b)$$

- Hence, NOR gate may be used to implement all three elementary operators.

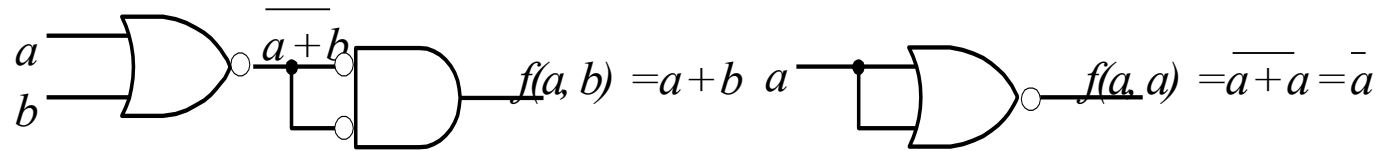
# Basic Functional Components

- AND, OR, and NOT gates constructed exclusively from NOR gates.



**OR gate**

**NOT gate**

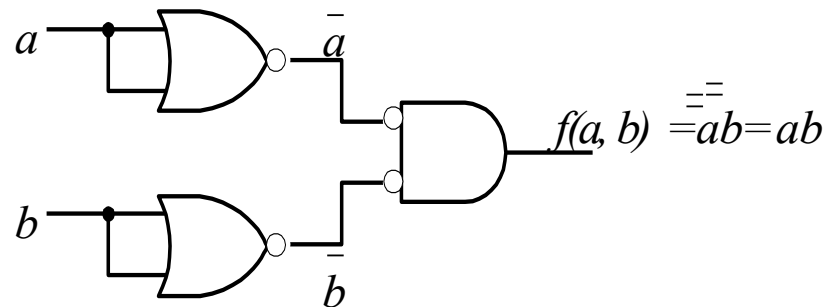

**AND gate**



# Basic Functional Components

- **Exclusive-OR (XOR)**

- $f_{\text{XOR}}(a, b) = a \oplus b = \bar{a}b + a\bar{b}$

| $a \ b$ | $f_{\text{XOR}}(a, b) = a \oplus b$ | $A \ B$ | $Y$ |
|---------|-------------------------------------|---------|-----|
| 0 0     | 0                                   | L L     | L   |
| 0 1     | 1                                   | L H     | H   |
| 1 0     | 1                                   | H L     | H   |
| 1 1     | 0                                   | H H     | L   |

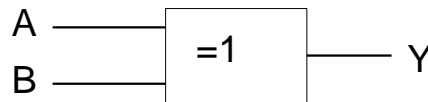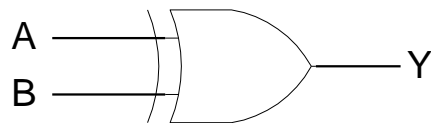(a) XOR logic function    (b) Electronic XOR gate



(c) Standard symbol    (d) IEEE block symbol

# Basic Functional Components

- POS of XOR

$$\begin{aligned}a \oplus b &= \bar{a}b + a\bar{b} \\&= \bar{a}a + \bar{a}b + a\bar{b} + b\bar{b} && [P2(a), P6(b)] \\&= \bar{a}(a + b) + \bar{b}(a + b) && [P5(b)] \\&= (\bar{a} + \bar{b})(a + b) && [P5(b)]\end{aligned}$$

- Some other useful relationships

- $a \oplus a = 0$  (2.25)
- $a \oplus \bar{a} = 1$  (2.26)
- $a \oplus 0 = a$  (2.27)
- $a \oplus 1 = \bar{a}$  (2.28)
- $\bar{a} \oplus \bar{b} = a \oplus b$  (2.29)
- $a \oplus b = b \oplus a$  (2.30)
- $a \oplus (b \oplus c) = (a \oplus b) \oplus c$  (2.31)

# Basic Functional Components (17)

- Output of XOR gate is asserted when the mathematical sum of inputs is *one*:

| $ab$ | $sum(a, b)$ | $sum(a, b) = 1?$ | $f(a, b) = a \oplus b$ |
|------|-------------|------------------|------------------------|
| 00   | 0           | False            | 0                      |
| 01   | 1           | True             | 1                      |
| 10   | 1           | True             | 1                      |
| 11   | 2           | False            | 0                      |

- The output of XOR is the *modulo-2* sum of its inputs.



# Basic Functional Components (18)

- **Exclusive-NOR (XNOR)**


- $f_{XNOR}(a, b) = \overline{a \oplus b} = a \odot b$

| $a$ | $b$ | $f_{XNOR}(a, b) = a \odot b$ |
|-----|-----|------------------------------|
| 0   | 0   | 1                            |
| 0   | 1   | 0                            |
| 1   | 0   | 0                            |
| 1   | 1   | 1                            |


(a)

| $A$ | $B$ | $Y$ |
|-----|-----|-----|
| L   | L   | H   |
| L   | H   | L   |
| H   | L   | L   |
| H   | H   | H   |

(b)

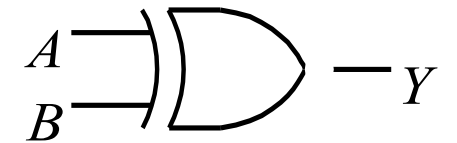

(c)

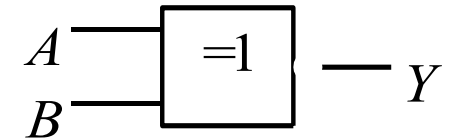

(d)


- (a) XNOR logic function
- (b) Electronic XNOR gate
- (c) Standard symbol
- (d) IEEE block symbol

# Analysis of Combinational Circuits (1)

- Digital Circuit **Design**:
  - Word description of a function
    - ⇒ a set of switching equations
    - ⇒ hardware realization (gates, programmable logic devices, etc.)
- Digital Circuit **Analysis**:
  - Hardware realization
    - ⇒ switching expressions, truth tables, timing diagrams, etc.
- Analysis is used
  - To determine the behavior of the circuit
  - To verify the correctness of the circuit
  - To assist in converting the circuit to a different form.
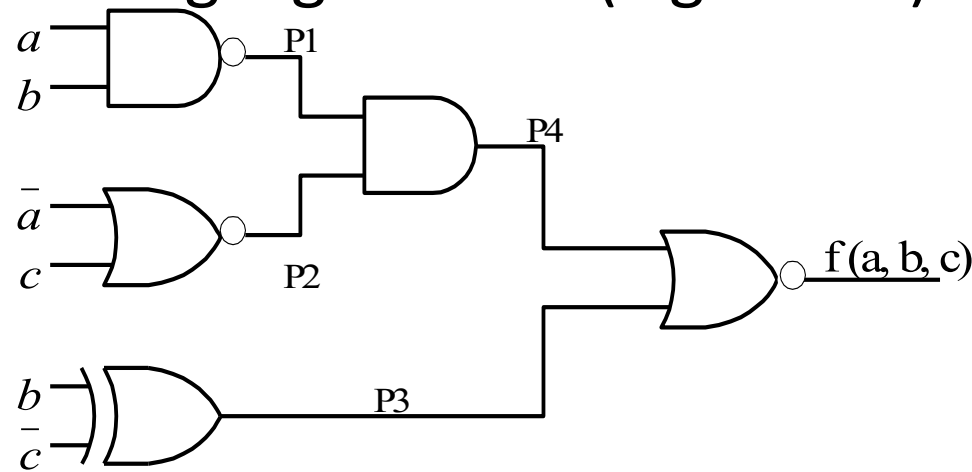
# Analysis of Combinational Circuits (2)


- **Algebraic Method:** Use switching algebra to derive a desired form.
- **Example 2.33:** Find a simplified switching expressions and logic network for the following logic circuit (Fig. 2.21a).



(a)

# Analysis of Combinational Circuits (4)

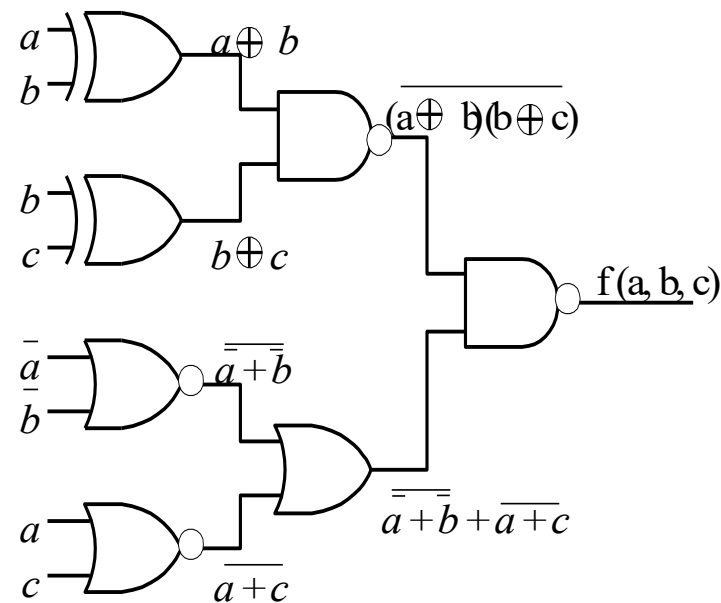- **Example 2.34:** Find a simplified switching expressions and logic network for the following logic circuit (Fig. 2.22).




Given circuit
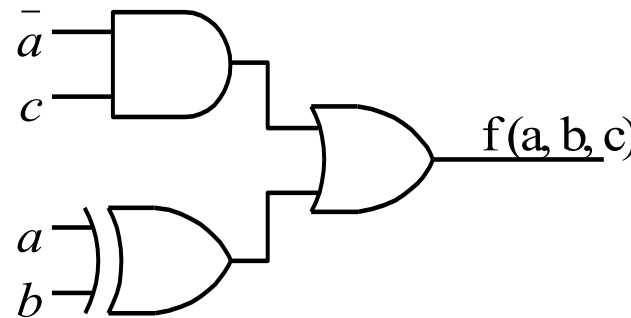
# Analysis of Combinational Circuits (5)

- Derive the output expression:

$$\begin{aligned} f(a,b,c) &= \overline{\overline{(a \oplus b)(b \oplus c)} \cdot (\overline{a+b} + \overline{a+c})} \\ &= \overline{\overline{(a \oplus b)(b \oplus c)} + \overline{a+b} + \overline{a+c}} \\ &= (a \oplus b)(b \oplus c) + (\overline{a+b})(a+c) \\ &= (a\overline{b} + \overline{a}b)(b\overline{c} + \overline{b}c) + (\overline{a+b})(a+c) \\ &= a\overline{b}\overline{b}\overline{c} + a\overline{b}bc + \overline{a}bb\overline{c} + \overline{a}b\overline{b}c + \overline{a}a + \overline{a}c + a\overline{b} + \overline{b}c \\ &= a\overline{b}\overline{c} + \overline{a}b\overline{c} + \overline{a}c + a\overline{b} + \overline{b}c \\ &= \overline{a}b\overline{c} + \overline{a}c + a\overline{b} + \overline{b}c \\ &= \overline{a}b\overline{c} + \overline{a}c + a\overline{b} \\ &= \overline{a}b + \overline{a}c + a\overline{b} \\ &= \overline{a}c + a \oplus b \end{aligned}$$



Simplified circuit

[T8(b)]  
[T8(a)]  
[Eq. 2.24]  
[P5(b)]  
[P6(b), T4(a)]  
[T4(a)]  
[T9(a)]  
[T7(a)]  
[Eq. 2.24]

# Analysis of Combinational Circuits (6)

- **Truth Table Method:** Derive the truth table one gate at a time.
- The truth table for Example 2.34:

| $abc$ | $\bar{a}c$ | $a \oplus b$ | $f(a,b,c)$ |
|-------|------------|--------------|------------|
| 000   | 0          | 0            | 0          |
| 001   | 1          | 0            | 1          |
| 010   | 0          | 1            | 1          |
| 011   | 1          | 1            | 1          |
| 100   | 0          | 1            | 1          |
| 101   | 0          | 1            | 1          |
| 110   | 0          | 0            | 0          |
| 111   | 0          | 0            | 0          |